

Experiment name:

Study of a clamper circuit.

Theory:

A Clamper Circuit is a circuit that adds a DC level to an AC signal. Clamper circuits consist of energy storage elements like capacitors. A simple clamper circuit comprises of a capacitor, a diode, a resistor and a dc battery if required. A Positive Clamper circuit is one that consists of a diode, a resistor and a capacitor and that shifts the output signal to the positive portion of the input signal. During the positive half cycle, the capacitor is charged to negative V_m while the diode gets forward biased and gets short circuited. A Negative Clamper circuit is one that consists of a diode, a resistor and a capacitor and that shifts the output signal to the negative portion of the input signal. During the negative half cycle, the diode gets reverse biased and gets open circuited.

Implements:

1. Resistor.
2. Diodes.
3. Connecting ware.
4. Oscilloscope.
5. Capacitor.

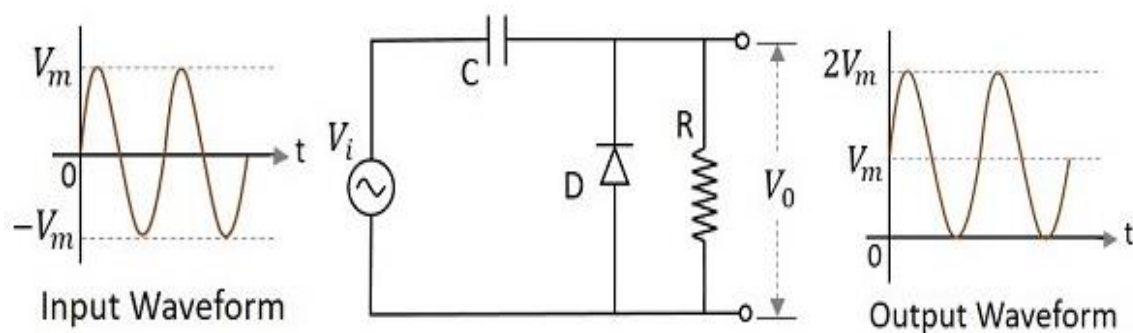
Diagram:

Figure: Positive clamper circuit


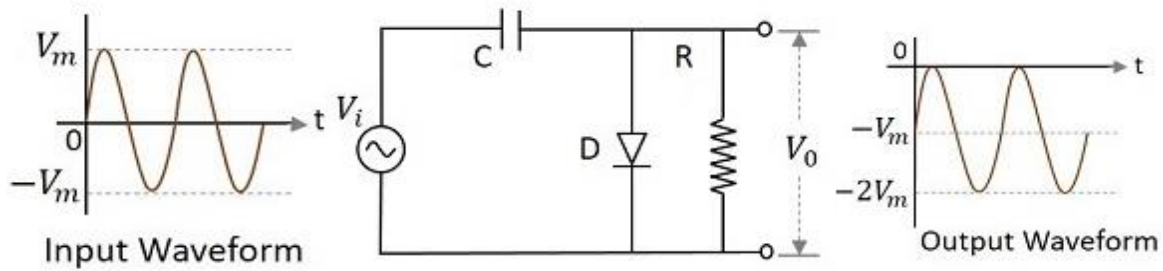
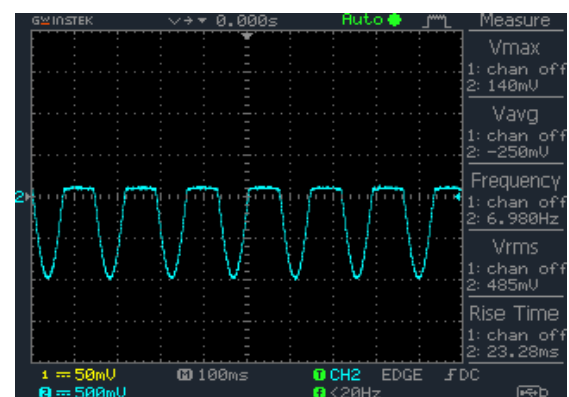
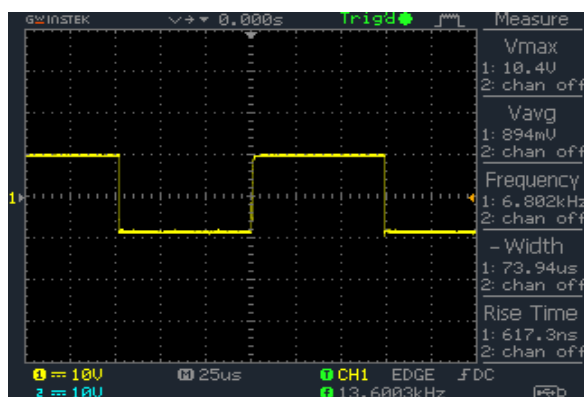
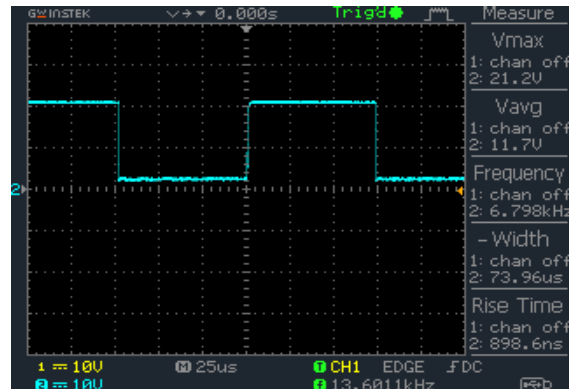


Figure: Negative clamper circuit

Figure:

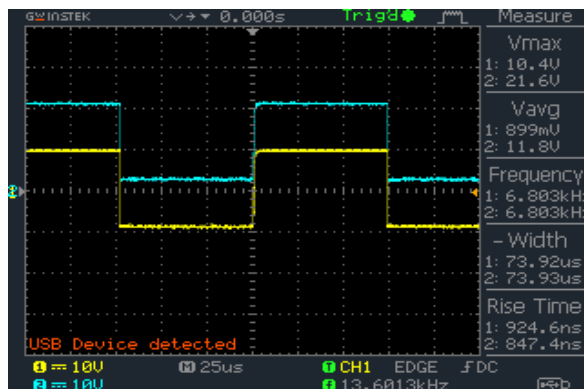

Conclusion:

Clipping is very widely used diode applications. In this experiment, we have constructed some clipper circuits, gave some input voltage and seen the output of the waveform in the oscilloscope.

