

# **BUBT**

## **Bangladesh University of Business & Technology**



### **Assignment On**

MUX and comparator

**Course Code:** CSE 205

**Course Title:** Digital Logic Design (DLD)

#### **Submitted By:**

Name: Syeda Nowshin Ibtat

ID: 17183103020

Intake: 39

Section: 01

Program: B.Sc. in CSE

#### **Submitted To:**

Name: Sohel Rana

Lecturer

Dept. of CSE


**Bangladesh University of Business &  
Technology**

**Date of Submission:** 28.12.19

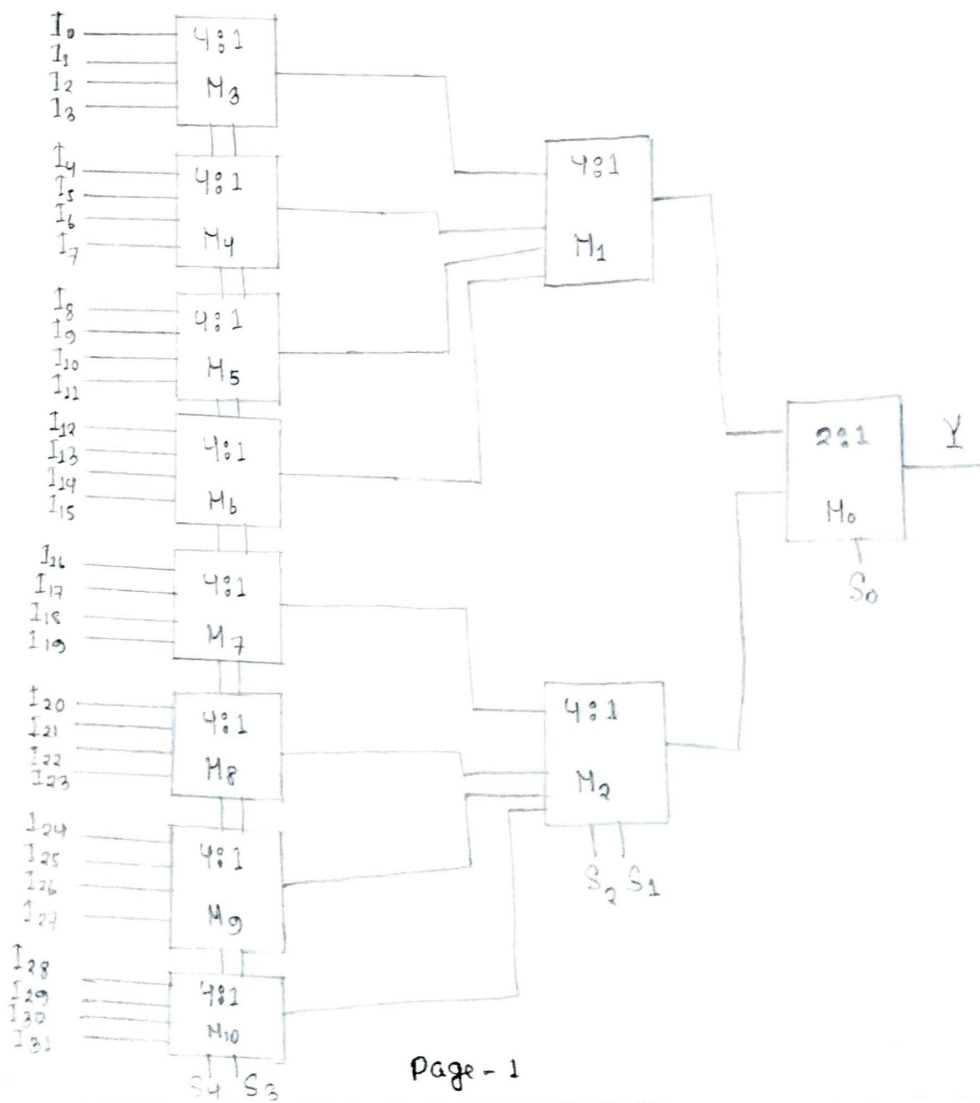Question 1: Design  $32 \times 1$  MUX using  $4 \times 1$  MUX.

Soln Soln: A multiplexer (or MUX), also known as a data selector, is a device that selects between several analog or digital input signals and forwards it to a single output line. Multiplexers are mainly used to increase the amount of data that can be sent over the network within a certain amount of time and bandwidth.


Now, designing  $32 \times 1$  MUX using  $4 \times 1$  MUX:



### Truth table:

$S_4$	$S_3$	$S_2$	$S_1$	$S_0$	Inputs (Y)	MUX
0	0	0	X	X	$I_0 - I_3$	$M_3$
0	0	1	X	X	$I_4 - I_7$	$\vdots$
0	1	0	X	X	$\vdots$	$\vdots$
0	1	1	X	X	$\vdots$	$\vdots$
1	0	0	X	X	$\vdots$	$\vdots$
$\vdots$	$\vdots$	$\vdots$	$\vdots$	$\vdots$	$\vdots$	$\vdots$
1	1	1	X	X	$I_{28} - I_{31}$	$M_{10}$

### Block Diagram :

 

Question: 02 Design 4-bit comparator.

Soln: A comparator is a combinational circuit that compare two numbers, A and B, and determine their relative magnitudes. The outcome of the comparison is specified by three binary variables that indicate whether  $A > B$ ,  $A = B$ , or  $A < B$ .

Now, Designing 4-bit comparator (magnitude):

Input?  
 $A = A_3A_2A_1A_0$   
 $B = B_3B_2B_1B_0$

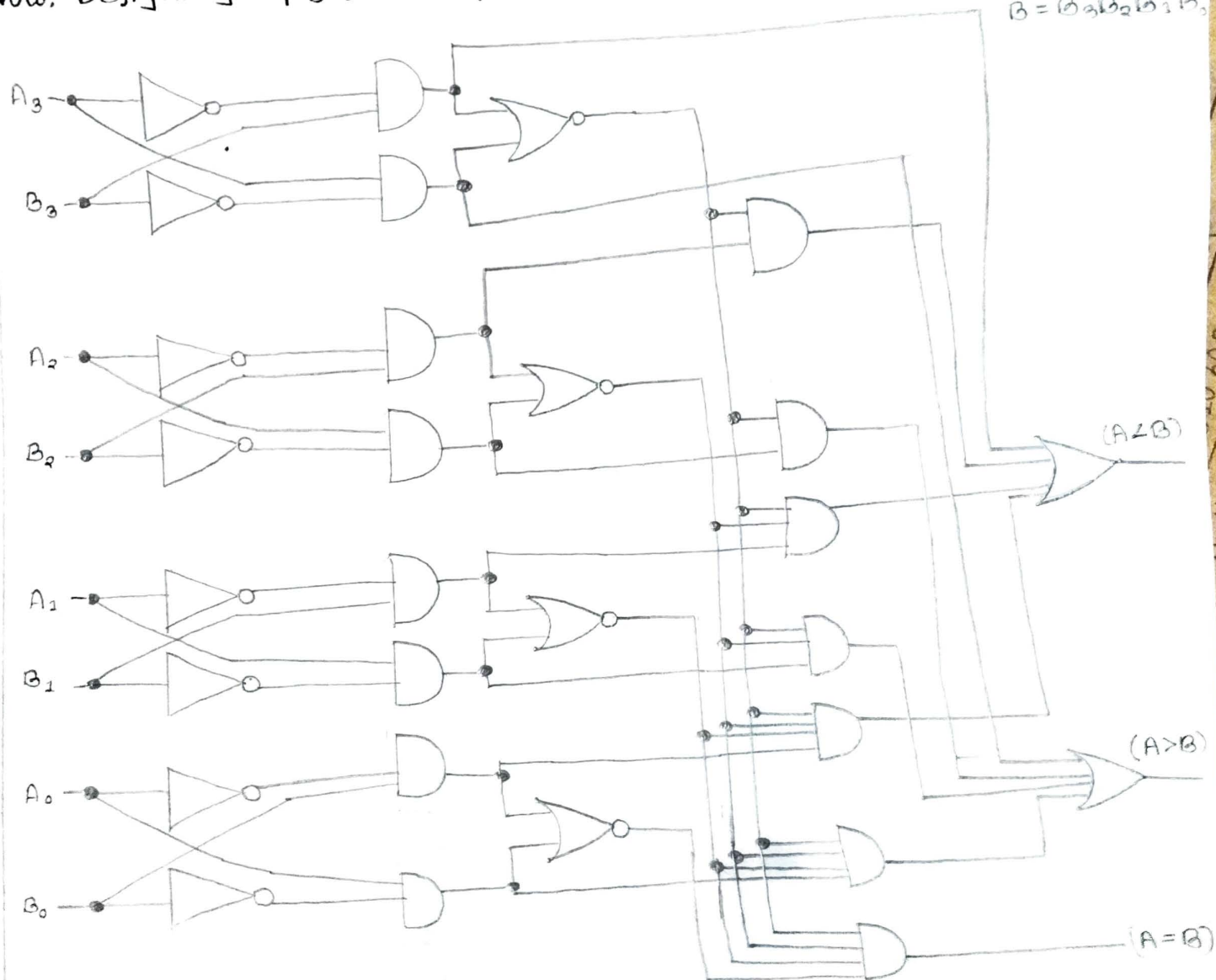


Figure: 4-bit magnitude comparator design

$$(1) A=B : A_3=B_3, A_2=B_2, A_1=B_1, A_0=B_0$$

$$X_i = A_i B_i + A_i' B_i'$$

$$\begin{aligned} \text{X-OR Invert} &= (A_i B_i' + A_i' B_i)' \\ &= (A_i' + B_i)(A_i + B_i') \\ &= A_i' A_i + A_i' B_i' + A_i B_i + B_i B_i' \\ &= A_i B_i + A_i' B_i' \end{aligned}$$

$$\underline{\text{output}} : X_3 \cdot X_2 \cdot X_1 \cdot X_0$$

$$(2) (A > B)$$

$$\underline{\text{output}} : A_3 B_3' + X_3 A_2 B_2' + X_3 X_2 A_1 B_1' + X_3 X_2 X_1 A_0 B_0'$$

$$(3) (A < B)$$

$$\underline{\text{Output}} : A_3' B_3 + X_3 A_2' B_2 + X_3 X_2 A_1' B_1 + X_3 X_2 X_1 A_0' B_0$$

Truth table :

COMPARING INPUTS				OUTPUT		
$A_3, B_3$	$A_2, B_2$	$A_1, B_1$	$A_0, B_0$	$A > B$	$A < B$	$A = B$
$A_3 > B_3$	X	X	X	H	L	L
$A_3 < B_3$	X	X	X	L	H	L
$A_3 = B_3$	$A_2 > B_2$	X	X	H	L	L
$A_3 = B_3$	$A_2 < B_2$	X	X	L	H	L
$A_3 = B_3$	$A_2 = B_2$	$A_1 > B_1$	X	H	L	L
$A_3 = B_3$	$A_2 = B_2$	$A_1 < B_1$	X	L	H	L
$A_3 = B_3$	$A_2 = B_2$	$A_1 = B_1$	$A_0 > B_0$	H	L	L
$A_3 = B_3$	$A_2 = B_2$	$A_1 = B_1$	$A_0 < B_0$	L	H	L
$A_3 = B_3$	$A_2 = B_2$	$A_1 = B_1$	$A_0 = B_0$	H	L	L
$A_3 = B_3$	$A_2 = B_2$	$A_1 = B_1$	$A_0 = B_0$	L	H	L
$A_3 = B_3$	$A_2 = B_2$	$A_1 = B_1$	$A_0 = B_0$	L	L	H

H = High Voltage, L = Low Voltage, Level, X = Don't care